

1152**Code : 15CS21T**Register
Number

--	--	--	--	--	--	--

II Semester Diploma Examination, Nov./Dec. 2017**DIGITAL AND COMPUTER FUNDAMENTALS****Time : 3 Hours |****| Max. Marks : 100**

- Note :** (i) Answer any **six** full questions from Part-A.
(ii) Answer any **seven** full questions from Part-B.

PART - A**I. Answer any six full questions :**

1. Explain binary number systems.
2. Write the Rules of Boolean algebra.
3. Construct the AND gate using NAND.
4. List the applications of multiplexer.
5. What is Flip-Flop ? Write the logical symbols of Flip-Flop.
6. List various applications of computers.
7. Compare ROM and RAM.
8. Write a short note on Inkjet Printer.
9. Define the following terms :
 - (i) Hardware
 - (ii) Software

BETA CONSOLE!

Diploma - [All Branches]

Beta Console Education

**5****5**

Diploma Question Papers [2015-19]

5

Beta Console Education

**5****5****5****5****5**

PART - B

II. Answer any **seven** questions :

10. Explain the terms :

10

(i) BCD

(ii) EBCDIC

(iii) ASCII Code

(iv) Gray Code

(v) Excess-3 Code

11. Convert the following :

10

(i) Binary to octal $(11010)_2$.(ii) Decimal to hexadecimal $(928)_{10}$.(iii) Binary to decimal $(11011)_2$.(iv) Octal to decimal $(146)_8$.(v) Hexadecimal to binary $(7AC)_{16}$.

12. State the Boolean laws with expressions.

10

13. Explain with a neat circuit and truth table of BCD to Decimal encoder.

10

14. Explain the working of 4-bit parallel-in-parallel-out (PIPO) shift register with logical circuit and truth table.

10

15. Explain 4-bit asynchronous ripple counter.

10

16. Draw a block diagram of computer system and explain.

10

17. Explain 'The working principles of keyboard'.

10

18. Draw the block diagram and explain the working principles of CRT.

10

19. List the advantages and disadvantages of optical disk.

10